

# Transmission Lines

Michael Brodskiy

Professor: E. Marengo Fuentes

September 18, 2023

- Transmission lines connect inputs to loads
  - $l$  is the length of the transmission lines
  - If  $l$  is not much smaller than  $\lambda$ , we need detailed analysis
  - If  $l$  is comparable to  $\lambda$ , then we can not use the lumped parameter model
  - We can, however, partition the transmission lines into segments where  $l \ll \lambda$ , then we can apply Kirchoff's circuit laws to each subdivided segment
  - For an imperfect dielectric, there is some loss
  - Some per unit-length properties:

1. Resistance per unit length:  $R'$  (ohm per meter)

$$R = R' \Delta z$$

2. Inductance per unit length:  $L'$  (Henry per meter)

$$L = L' \Delta z$$

3. Capacitance per unit length:  $C'$  (Farad per meter)

$$C = C' \Delta z$$

4. Conductance per unit length:  $G'$  (Siemens per meter)

$$G = G' \Delta z$$

- Using this, we obtain the Helmholtz Equation:

$$\frac{d^2 \tilde{V}(z)}{dz^2} - \gamma^2 \tilde{V}(z) = 0$$

- Where  $\gamma = \sqrt{(j\omega C' + G')(j\omega L' + R')}$

- For a Unidimensional Wave Equation:

- The characteristic equation becomes:  $m^2 - \gamma^2 = 0 \rightarrow m = \pm\gamma$
- The solutions to the above differential equation are superpositions of  $\{e^{\gamma z}, e^{-\gamma z}\}$
- $\gamma = \sqrt{(R' + j\omega L')(G' + j\omega C')}$ , where:
  - \*  $R'$  is the resistance per unit length
  - \*  $L'$  is the impedance per unit length
  - \*  $j = \sqrt{-1}$
  - \*  $\gamma = R_e\gamma + I_m\gamma$
  - \*  $R_e\gamma = \alpha$ , the attenuation constant
  - \*  $I_m\gamma = \beta$ , the phase constant (sometimes, notation used is  $k = \beta$ , like the wave number)

$$\tilde{V}(z) = V_o^+ e^{-\gamma z} + V_o^- e^{\gamma z}$$

- We know from the definitions above that  $\gamma = \alpha + j\beta$
- For  $\alpha > 0$ , we are dealing with a (passive) lossy material ( $\alpha = 0$ ) is a loss less material
- For  $\alpha < 0$ , we are dealing with a gainy material
- The wave coming from the source is known as the “incident” wave, and the wave coming from the load is known as “reflected”

$$-\frac{dV}{dz} = (R' + j\omega L')\tilde{I}(z)$$

- Solving this by incorporation the equation for  $\tilde{V}$  above, we obtain:

$$\tilde{I} = (V_o^+ e^{-\gamma z} - V_o^- e^{\gamma z}) \left( \frac{\gamma}{R' + j\omega L'} \right)$$

- We then define  $z_o = \frac{R' + j\omega L}{\gamma}$  as our characteristic impedance:

$$\tilde{I} = \frac{1}{z_o} (V_o^+ e^{-\gamma z} - V_o^- e^{\gamma z})$$

- There are thus two unknowns:  $V_o^+$ , which depends on source, and  $V_o^-$ , which is the reflected wave amplitude (depends on load)
  - \* The incident wave (in phase domain):  $\tilde{V} = V_o^+ e^{-\alpha z} e^{-j\beta z}$
  - \* In time domain, this becomes:  $v(z, t) = |V_o^+| e^{-\alpha z} \cos(\omega t - \beta z + \phi_+)$ <sup>1</sup>

---

<sup>1</sup> $\beta$  represents the wave number

- For a lossless line ( $R' = 0, G' = 0$ , and a pure inductor and capacitor)

$$\gamma = \sqrt{(jC'\omega)(jL'\omega)} \rightarrow \beta = \omega\sqrt{L'C'} = \frac{\omega}{U_{ph}}$$

$$U_{ph} = \frac{1}{\sqrt{L'C'}} = \frac{1}{\sqrt{\mu\varepsilon}} = c \text{ in dielectric}$$

- The reflection coefficient ( $\Gamma$ ) is given by:

$$\Gamma = \frac{V_o^-}{V_o^+}$$

$$V_{load} = V_o^+(1 + \Gamma)$$

$$I_{load} = \frac{V_o^+}{z_o}(1 - \Gamma)$$

- The normalized load impedance:  $\hat{z}_L = \frac{z_L}{z_o}$

$$\Gamma = \frac{z_l - z_o}{z_l + z_o} \rightarrow \Gamma = \frac{\hat{z}_L - 1}{\hat{z}_L + 1}$$

- Special Cases:

- \* Short Circuit:

$$\Gamma_{sc} = -1$$

- \* Open Circuit:

$$\Gamma_{oc} = 1$$

- Reactive load, no real absorption

- A Phase-Shifted  $\Gamma$  would look as follows:

$$\Gamma_l = \left( \frac{z_L - z_o}{z_L + z_o} \right) e^{-j(2\beta l)}$$

- Standing Waves

- $\tilde{V}(d) = V_o^+ e^{-j\beta d} + V_o^+ \Gamma e^{j\beta d}$

$$|\tilde{V}(d)| = |V_o^+| [1 + |\Gamma|^2 + 2|\Gamma| \cos(2\beta d - \theta_r)]^{\frac{1}{2}}$$

- \* This fluctuates between a minimum ( $V_{min}$ ) and maximum ( $V_{max}$ ) value

- \* Maximum/minimum possible value is determined by the cos term and is  $\pm 2|\Gamma|$

- From the formula for  $\Gamma$ , we see that  $\Gamma = 0$  when the load impedance matches the internal impedance

- \* This is known as load matching

- Thus, when  $\Gamma = 0$ , we know  $|\tilde{V}(d)| = |V_0^+|$
- The standing wave ratio is defined as follows:

$$SWR = \frac{1 + |\Gamma|}{1 - |\Gamma|}$$

- This measures the matching level of load to the line; ideally,  $\Gamma = 0$ , and  $SWR = 1$ ; worst case,  $|\Gamma| = 1$ , and  $SWR = \infty$
- In reference to the maximums and minimums, these occur when  $2\beta d - \theta_r = 2n\pi$  and  $2\beta d - \theta_r = (2n + 1)\pi$ , respectively. This results in:

$$\begin{cases} d_{max} = \frac{2n\pi + \theta_r}{2\beta} \\ d_{min} = \frac{(2n + 1)\pi + \theta_r}{\beta} \end{cases}$$