

Transmission Lines

Michael Brodskiy

Professor: E. Marengo Fuentes

September 14, 2023

- Transmission lines connect inputs to loads
 - l is the length of the transmission lines
 - If l is not much smaller than λ , we need detailed analysis
 - If l is comparable to λ , then we can not use the lumped parameter model
 - We can, however, partition the transmission lines into segments where $l \ll \lambda$, then we can apply Kirchoff's circuit laws to each subdivided segment
 - For an imperfect dielectric, there is some loss
 - Some per unit-length properties:

1. Resistance per unit length: R' (ohm per meter)

$$R = R' \Delta z$$

2. Inductance per unit length: L' (Henry per meter)

$$L = L' \Delta z$$

3. Capacitance per unit length: C' (Farad per meter)

$$C = C' \Delta z$$

4. Conductance per unit length: G' (Siemens per meter)

$$G = G' \Delta z$$

- Using this, we obtain the Helmholtz Equation:

$$\frac{d^2 \tilde{V}(z)}{dz^2} - \gamma^2 \tilde{V}(z) = 0$$

- Where $\gamma = \sqrt{(j\omega C' + G')(j\omega L' + R')}$

- For a Unidimensional Wave Equation:

- The characteristic equation becomes: $m^2 - \gamma^2 = 0 \rightarrow m = \pm\gamma$
- The solutions to the above differential equation are superpositions of $\{e^{\gamma z}, e^{-\gamma z}\}$
- $\gamma = \sqrt{(R' + j\omega L')(G' + j\omega C')}$, where:
 - * R' is the resistance per unit length
 - * L' is the impedance per unit length
 - * $j = \sqrt{-1}$
 - * $\gamma = R_e\gamma + I_m\gamma$
 - * $R_e\gamma = \alpha$, the attenuation constant
 - * $I_m\gamma = \beta$, the phase constant (sometimes, notation used is $k = \beta$, like the wave number)

$$\tilde{V}(z) = V_o^+ e^{-\gamma z} + V_o^- e^{\gamma z}$$

- We know from the definitions above that $\gamma = \alpha + j\beta$
- For $\alpha > 0$, we are dealing with a (passive) lossy material ($\alpha = 0$) is a loss less material
- For $\alpha < 0$, we are dealing with a gainy material
- The wave coming from the source is known as the “incident” wave, and the wave coming from the load is known as “reflected”

$$-\frac{dV}{dz} = (R' + j\omega L')\tilde{I}(z)$$

- Solving this by incorporation the equation for \tilde{V} above, we obtain:

$$\tilde{I} = (V_o^+ e^{-\gamma z} - V_o^- e^{\gamma z}) \left(\frac{\gamma}{R' + j\omega L'} \right)$$

- We then define $z_o = \frac{R' + j\omega L}{\gamma}$ as our characteristic impedance:

$$\tilde{I} = \frac{1}{z_o} (V_o^+ e^{-\gamma z} - V_o^- e^{\gamma z})$$

- There are thus two unknowns: V_o^+ , which depends on source, and V_o^- , which is the reflected wave amplitude (depends on load)
 - * The incident wave (in phase domain): $\tilde{V} = V_o^+ e^{-\alpha z} e^{-j\beta z}$
 - * In time domain, this becomes: $v(z, t) = |V_o^+| e^{-\alpha z} \cos(\omega t - \beta z + \phi_+)$ ¹

¹ β represents the wave number

- For a lossless line ($R' = 0, G' = 0$, and a pure inductor and capacitor)

$$\gamma = \sqrt{(jC'\omega)(jL'\omega)} \rightarrow \beta = \omega\sqrt{L'C'} = \frac{\omega}{U_{ph}}$$

$$U_{ph} = \frac{1}{\sqrt{L'C'}} = \frac{1}{\sqrt{\mu\varepsilon}} = c \text{ in dielectric}$$

- The reflection coefficient (Γ) is given by:

$$\Gamma = \frac{V_o^-}{V_o^+}$$

$$V_{load} = V_o^+(1 + \Gamma)$$

$$I_{load} = \frac{V_o^+}{z_o}(1 - \Gamma)$$

- The normalized load impedance: $\hat{z}_L = \frac{z_L}{z_o}$

$$\Gamma = \frac{z_l - z_o}{z_l + z_o} \rightarrow \Gamma = \frac{\hat{z}_L - 1}{\hat{z}_L + 1}$$

- Special Cases:

- * Short Circuit:

$$\Gamma_{sc} = -1$$

- * Open Circuit:

$$\Gamma_{oc} = 1$$

- Reactive load, no real absorption

- A Phase-Shifted Γ would look as follows:

$$\Gamma_l = \left(\frac{z_L - z_o}{z_L + z_o} \right) e^{-j(2\beta l)}$$